
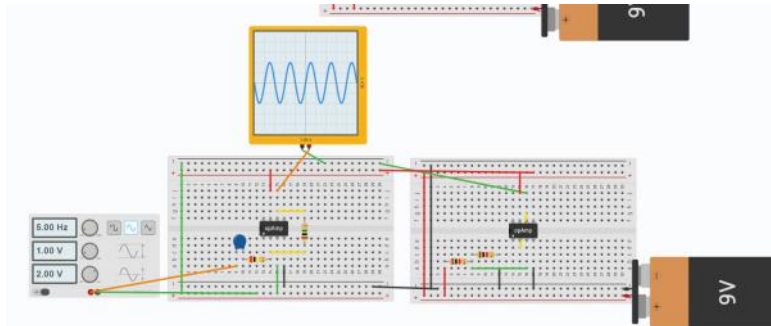
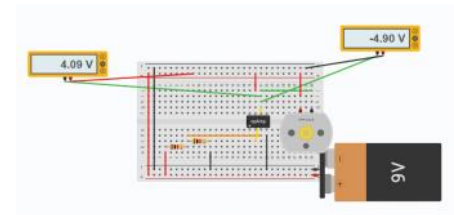

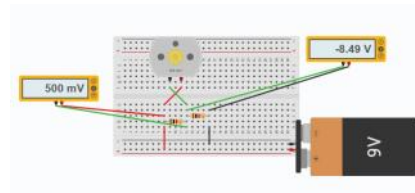
## Week 7: More Circuits Lab

Monday, October 10, 2022 10:57 AM

No OP AMP DC Motor: Voltage Drop: 500mV, 999RPM  
OP AMP DC Motor: Voltage Drop 4.09V, 8174RPM




### High pass filter design

**Report measured values of resistors and capacitors, not "labeled" values**

- Resistor on input: 14.6 k $\Omega$
- Feedback resistor: 99.7 k $\Omega$
- Capacitor: 2.17  $\mu$ F

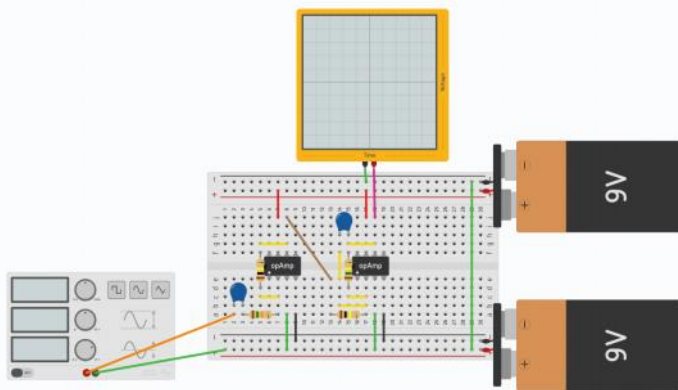**Calculations using measured values**

- Gain: 16.7 dB
- Cutoff frequency: 5.02 Hz



### Low pass filter design

**Report measured values of resistors and capacitors, not "labeled" values.**


- Resistor on input: 100 k $\Omega$
- Feedback resistor: 144 k $\Omega$
- Capacitor: 22.2 nF

**Calculations using measured values**

- Gain: 3.17 dB
- Cutoff frequency: 49.8 Hz


### Circuit

- Calculated overall gain: 19.9 dB

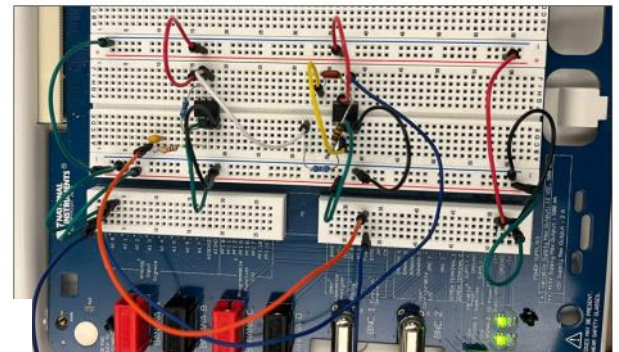
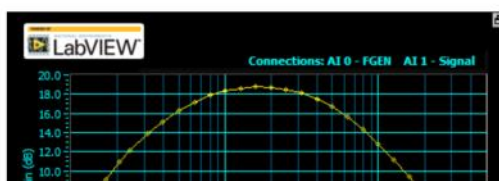
### Bode plot (gain vs frequency only)

- Approximate maximum gain according to Bode plot: 18.8 dB
- Approximate band and pass range according to Bode plot: 5.03 Hz to 50.1 Hz



## Bode plot (gain vs frequency only)

- Approximate maximum gain according to Bode plot: 18.8 dB
- Approximate band and pass range according to Bode plot: 5.03 Hz to 50.1 Hz



## Week 8: EKG Project

### Objectives:

1. Construct a working instrumentation amplifier circuit on your solderless breadboard to measure your ECG signal
  - You will use 2 batteries for this, so you don't have to worry about building a voltage follower
  - Measure your ECG using the ELVIS boards and the ELVIS tool "Dynamic Signal Analyzer"
  - No filtering is needed yet, just the instrumentation amp part
2. Design the voltage follower and instrumentation amp part of the ECG in Fusion 360 - just get the schematic done
3. Prepare for week 9 and do the presentation work.